

# ADVANCED CONTROL DESIGN TECHNIQUES FOR POWER CONVERTERS(EE608)

## TOPIC: CURRENT MODE CONTROL IN BUCK CONVERTER

FACULTY

DR. A.V. RAVITEJA

2023EEM1050

2023EEM1051

STUDENT

(SHIVAM SAINI )

(SHUBHAM FAUJDAR)

# BUCK CONVERTER CURRENT MODE CONTROL

---

Objective 1: Simulate a closed loop buck converter with current mode control

Objective 2: Obtain the bode plot before and after the controller design and show that a phase margin of 35 degrees is achieved.

Objective 3: Draw the nyquist plot of open loop gain and confirm the same as in 2

Objective 4: Draw the root-locus of the inductor series resistance variation and show the limits of the inductor series resistance variation for stable operation.

# CALCULATIONS

---

$$f = 100\text{KHz}$$

$$V_i = 48\text{V}$$

$$V_o = 12\text{V}$$

$$\Delta V_o / V_o = 0.05$$

$$R = 15\Omega$$

$$L = 100\mu\text{H}$$

$$C = 26\mu\text{F}$$

$$D = 0.25$$

$$\Delta i_L = 2\%$$

$$\Delta V_o = 5\%$$

*Outer loop*

$$K_p = 0.08$$

$$K_i = 704.03$$

*Inner loop*


$$K_p = 0.009$$

$$K_i = 50.90$$


❖ Inner loop is faster than outer loop.

❖ Some tolerance is also considered.


# BLOCK DIAGRAM

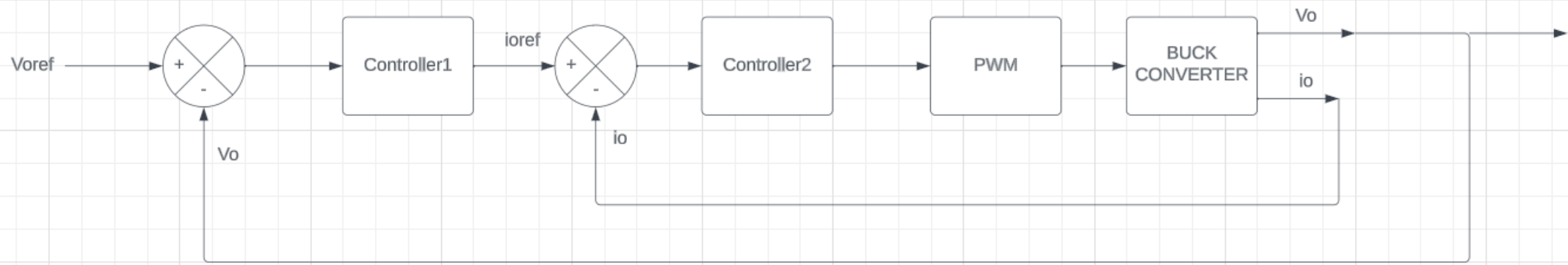

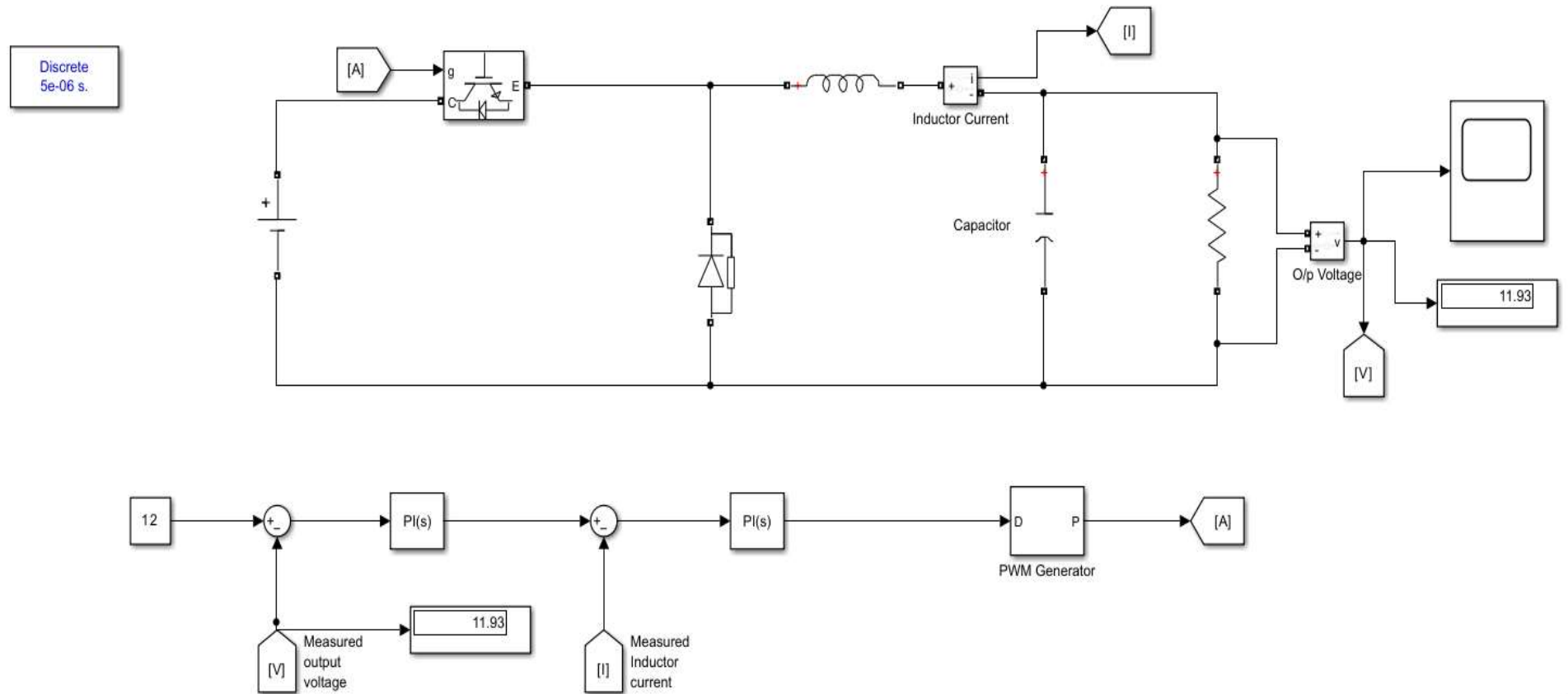1. Simulate a closed loop buck converter with current mode control
2. Obtain the bode plot before and after the controller design and show that a phase margin of 35 degrees is achieved.
3. Draw the nyquist plot of open loop gain and confirm the same as in 2
4. Draw the root-locus of the inductor series resistance variation and show the limits of the inductor series resistance variation for stable operation.



# Output Voltage

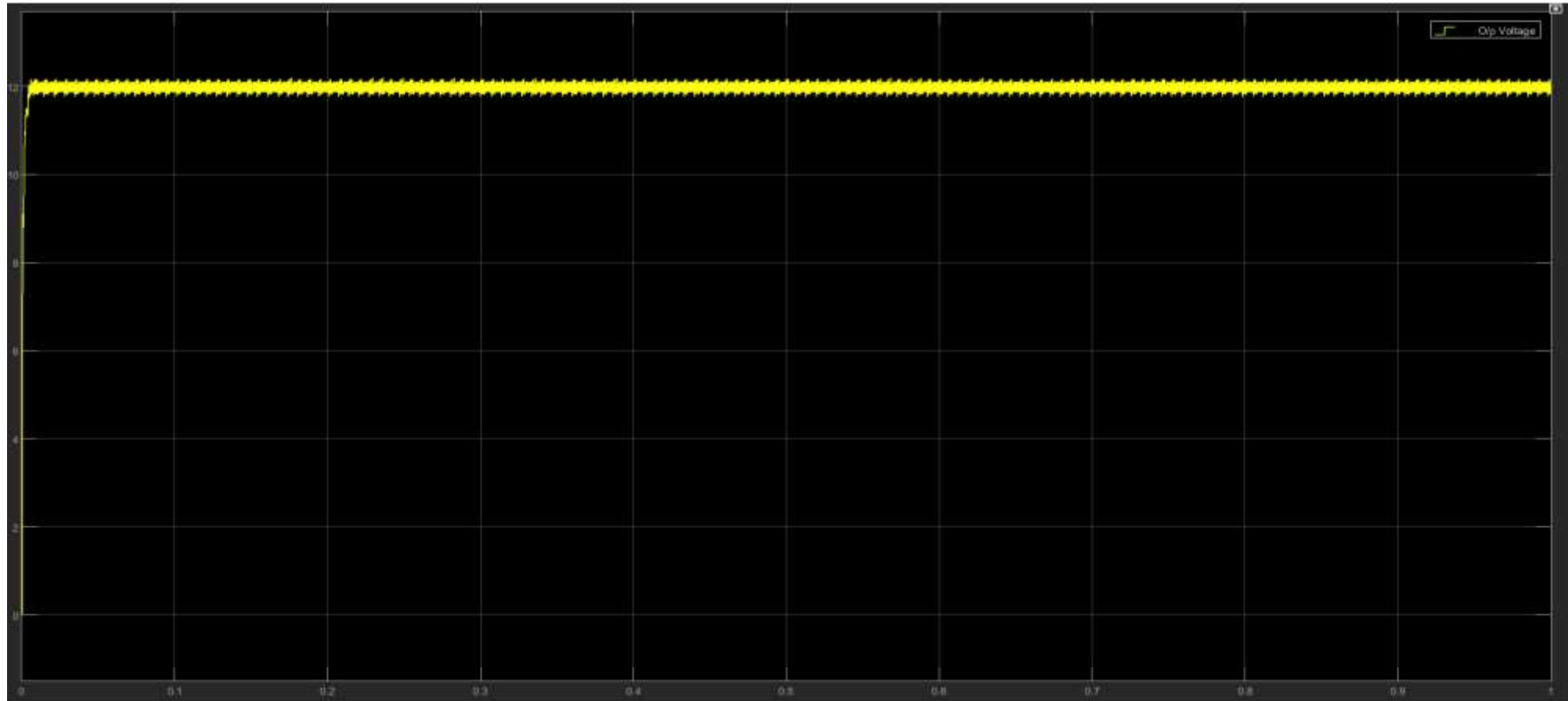

# MATLAB CODE FOR FINDING PHASE MARGIN Without Controller

---


```
clear all;clc;
Vdc=48;
R=15;
L=100e-6;
C=25e-6;
n = [Vdc/L Vdc/(R*L*C)];
d=[ 1 1/(R*C) 1/(L*C)];
t = tf(n,d);    %(iL/d) wo PI
n_1=[Vdc/(L*C)];
d_1=[1 1/(R*C) 1/(L*C)];
t_1=tf(n_1,d_1);    % Vo/d wo PI
disp('\n Transfer Function without PI controller:');
flag= (t_1)/t    % Vo/iL wo PI
```

\n Transfer Function without PI controller:

flag =

$$\frac{1.92e10 s^2 + 5.12e13 s + 7.68e18}{480000 s^3 + 2.56e09 s^2 + 1.954e14 s + 5.12e17}$$

Continuous-time transfer function.

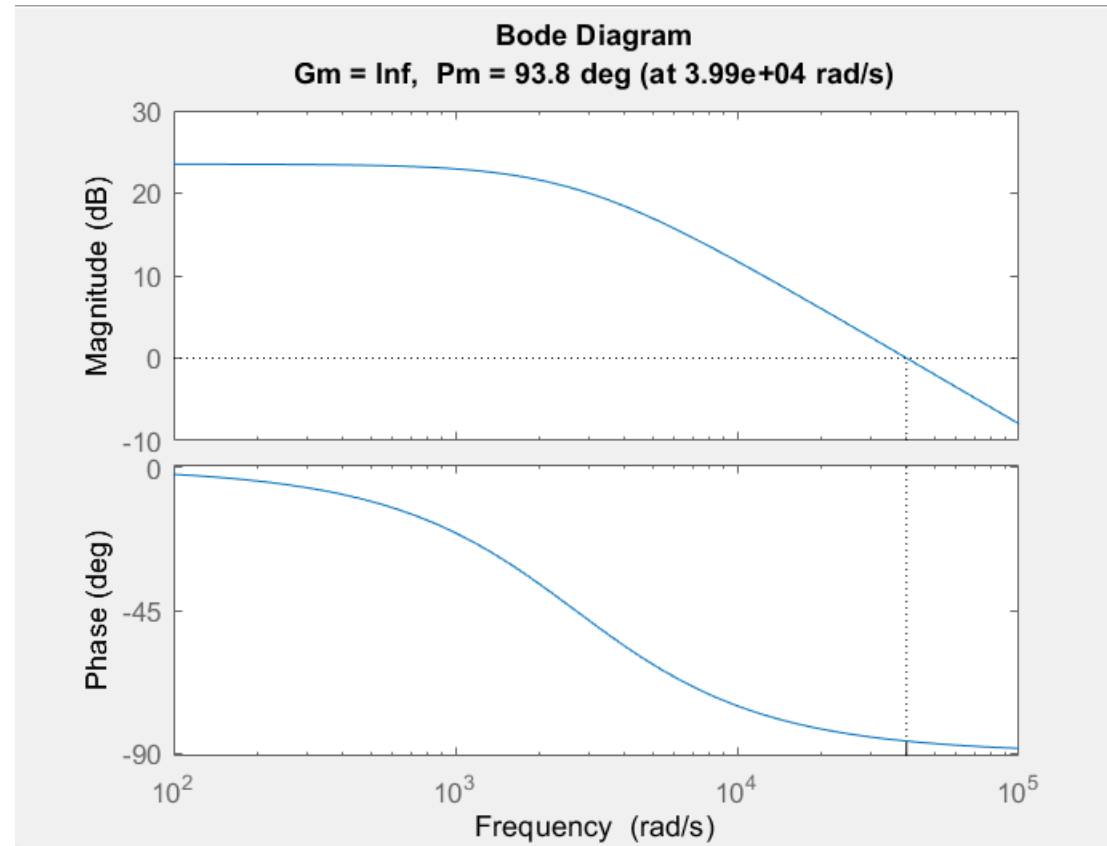





# MATLAB CODE FOR FINDING PHASE MARGIN With Controller

---


```
kp_i= [0.0009];  
a=50.90;  
m = [1 0];  
ki_i= a*tf(1,m);  
c= kp_i+ki_i;  
t_11=t*c;    %iL/d w PI inner loop  
In= t_11/(t_11+1);  
kp_o= [0.08];  
p =704.03;  
m_1 = [1 0];  
ki_2= p*tf(1,m_1);  
c_2= kp_o+ki_2;  
disp('\n Transfer function after adding PI contoller:')  
flag_2= (In*c_2)  
%margin(flag_2);  
%pzplot(flag_2)  
%nyquist(flag_2)  
%r=0.005:0.02:1
```

flag\_2 =

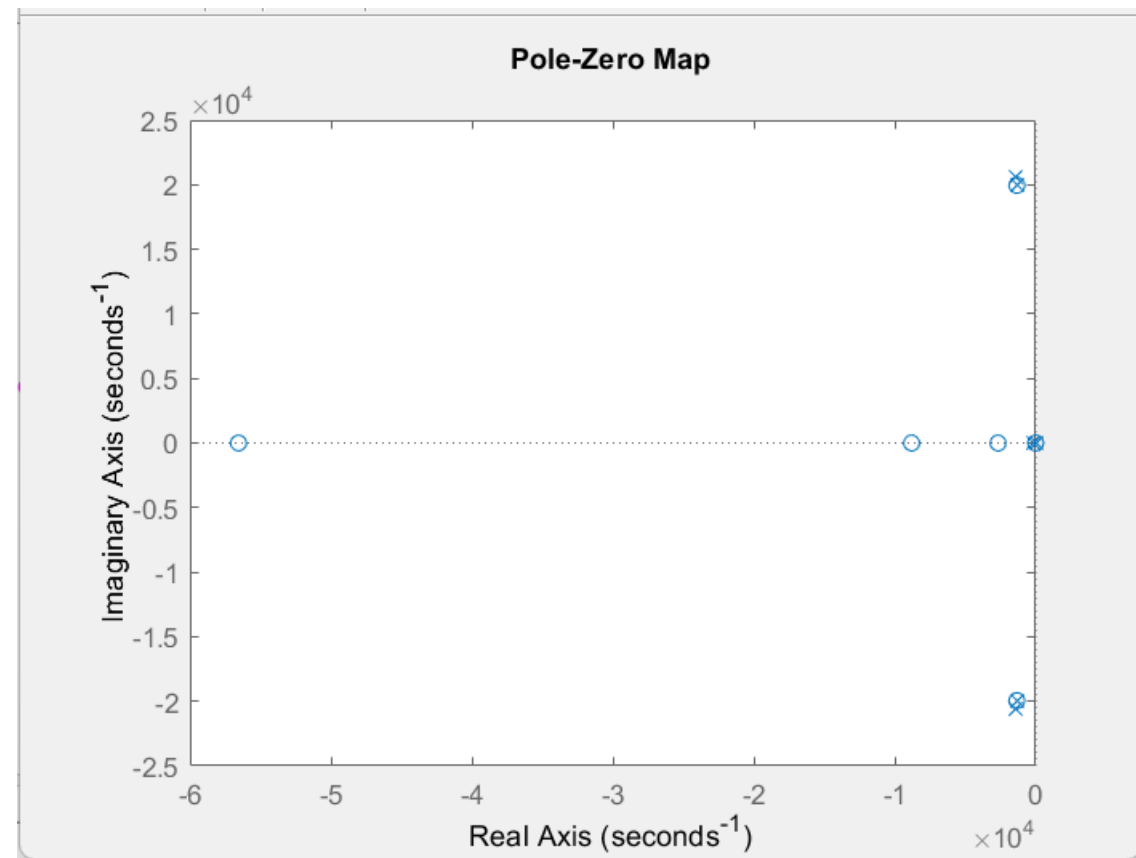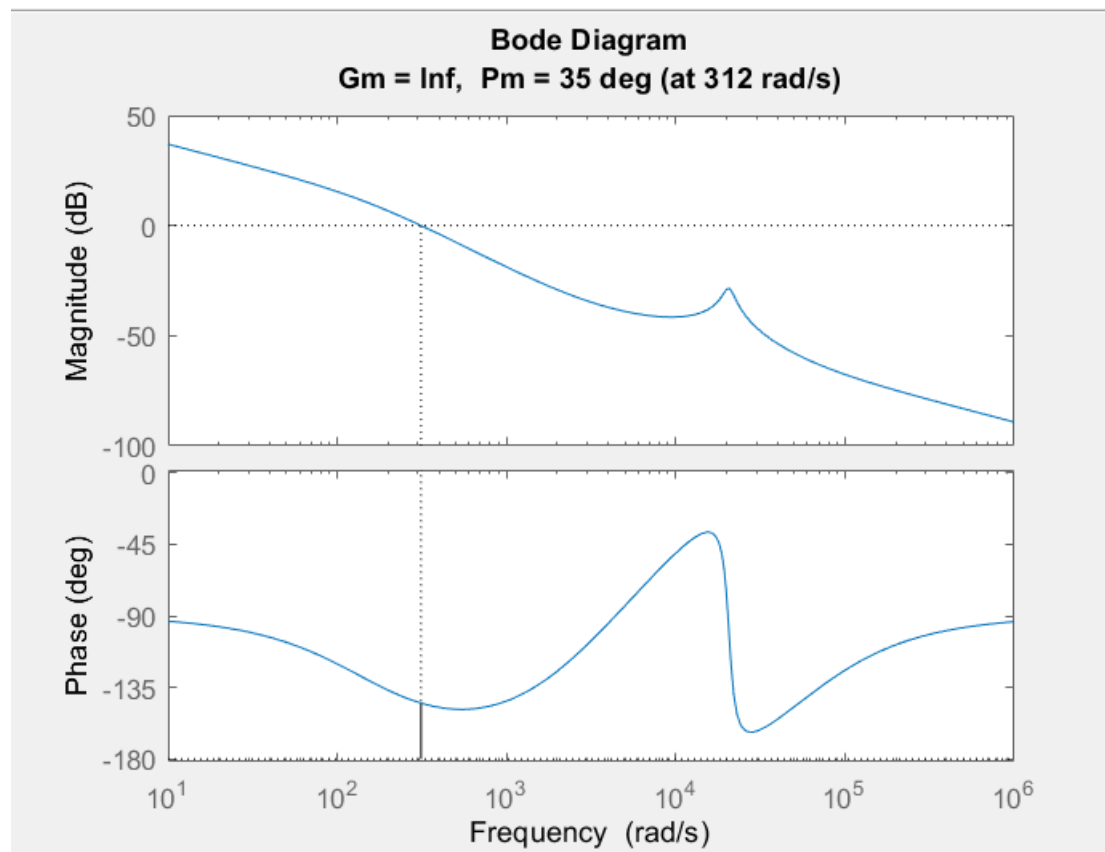
$$\frac{34.56 s^6 + 2.443e06 s^5 + 4.332e10 s^4 + 1.048e15 s^3 + 9.412e18 s^2 + 1.835e22 s}{s^7 + 5765 s^6 + 8.338e08 s^5 + 2.44e12 s^4 + 1.704e17 s^3 + 2.606e19 s^2}$$




Nyquist Diagram

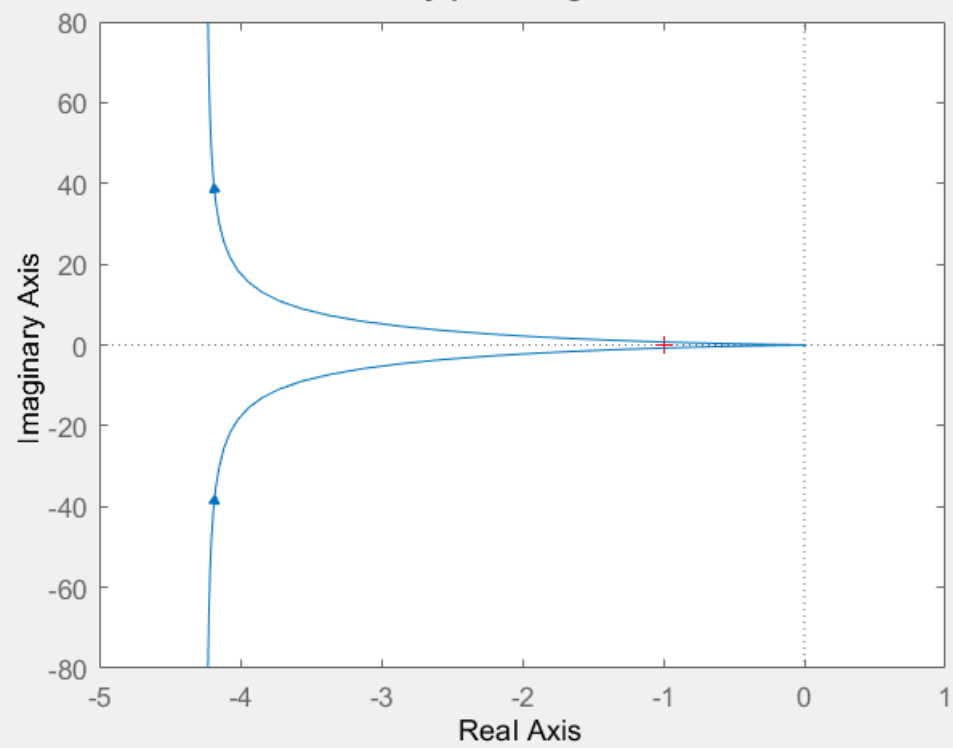

Nyquist Diagram

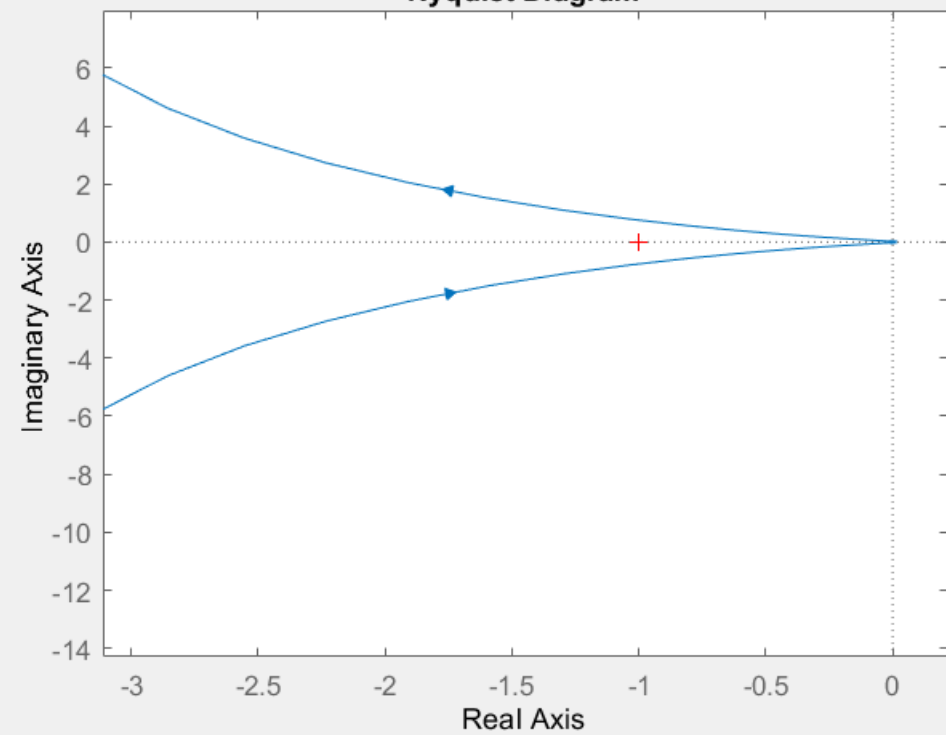

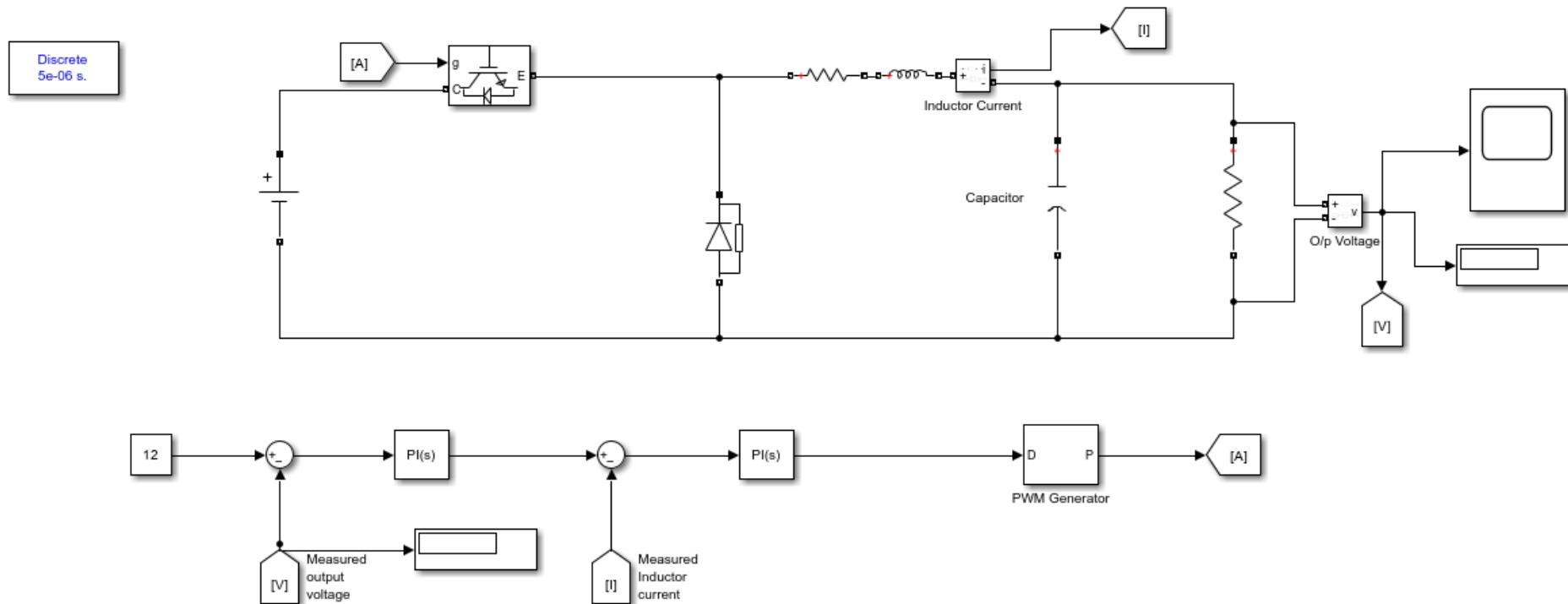Draw the root-locus of the inductor series Resistance variation and show the limits of the inductor series resistance variation for stable operation.



\n Transfer Function of  $i_L/d$ ::

$V_{dc}$

---


$$C L R \left| \frac{1}{s^2} + \frac{r}{L} + \frac{1}{C R} \right| s + \frac{1}{C L} + \frac{r}{C L R} \left| \right|$$

\n Transfer function of open loop:

$$V_{dc} (k_i + k_p s) \left| \frac{k_{ii}}{s} \right|$$


---

$$V_{dc} k_i + R s^2 + r s + L s^3 + V_{dc} k_p s + C L R s^3 + C R r s^2$$

Expression with "r" factored out from the denominator:

$$\frac{V_{dc} k_i k_{ii} + V_{dc} k_p k_{pp} s^2 + V_{dc} k_{ii} k_p s + V_{dc} k_i k_{pp} s}{(C R s^3 + s^2) r + L s^3 + R s^2 + V_{dc} k_i s + V_{dc} k_p s^2 + C L R s^4}$$

```



Num = [(R*C) 1 0 0];
den = [(R*L*C) L R (Vdc*(kp_i)) (Vdc*(a)) 0];
disp('\n Transfer function with controller::');
pop_tf(Num,den)
rlocus(pop);

```

```

kp_i=1; %kp inner
a=10; %ki inner

```

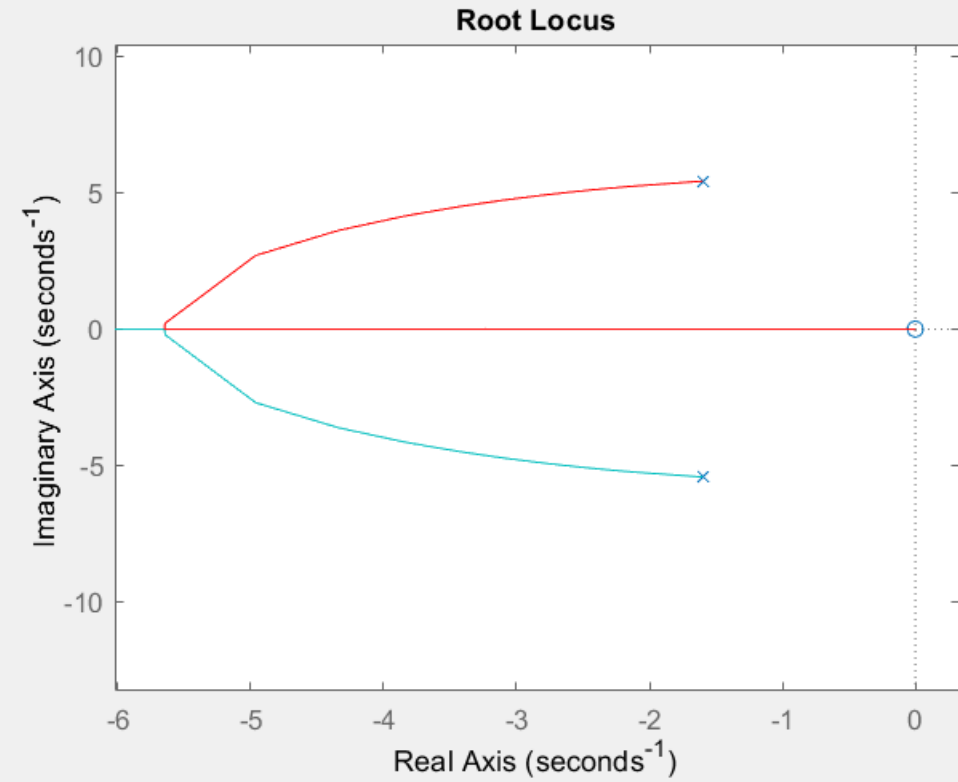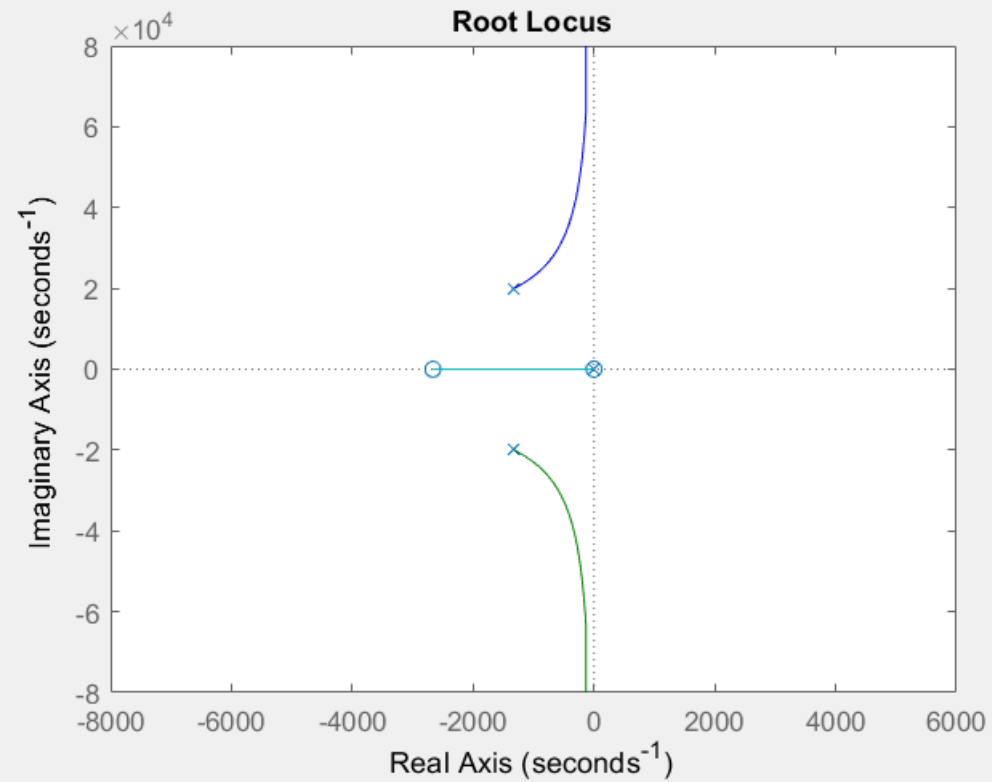


---


# EXTRA TASKS




# SHORT CIRCUIT

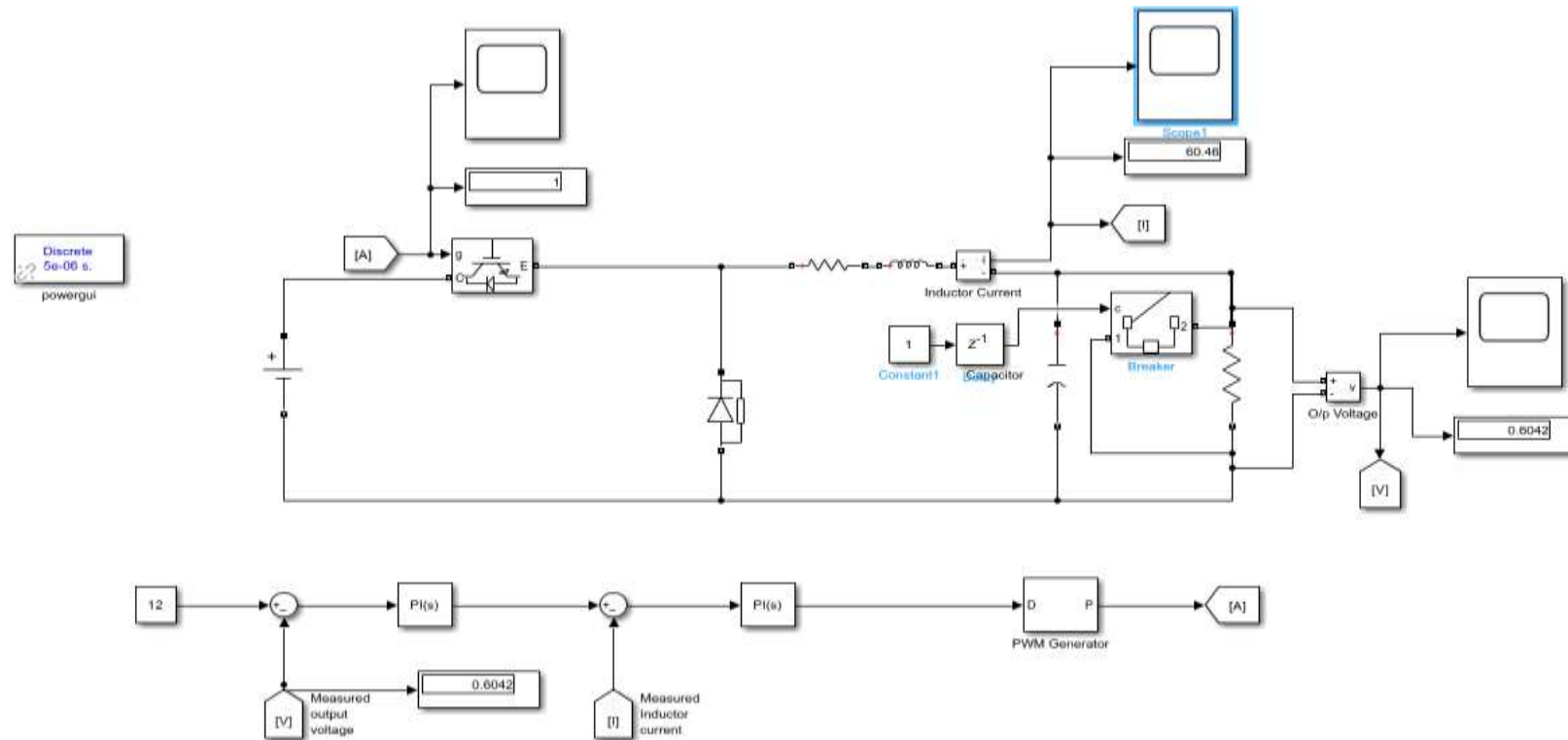



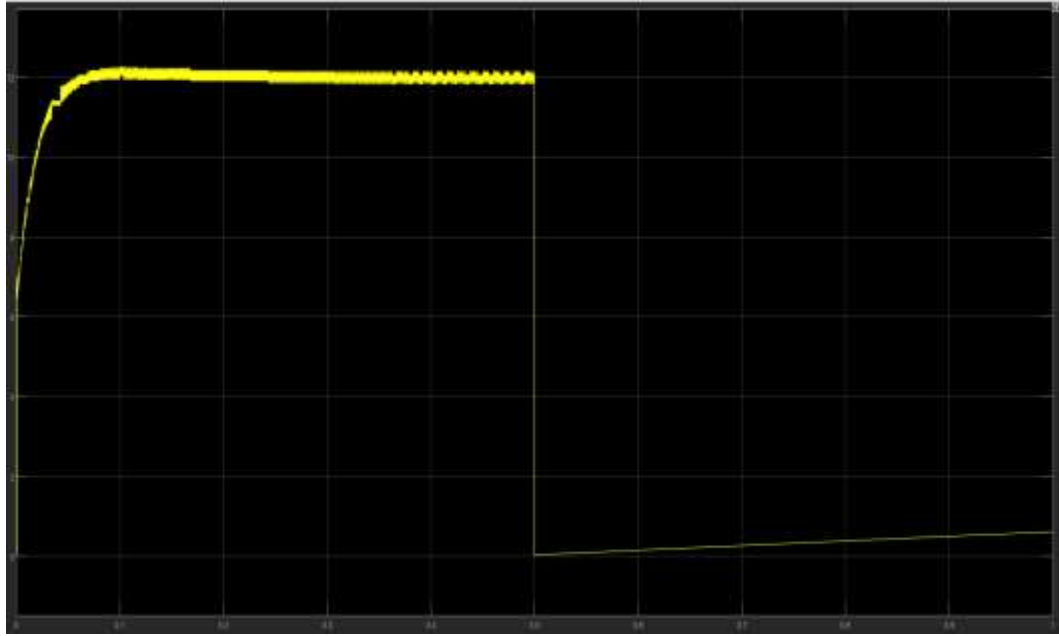



*Voltage Profile*

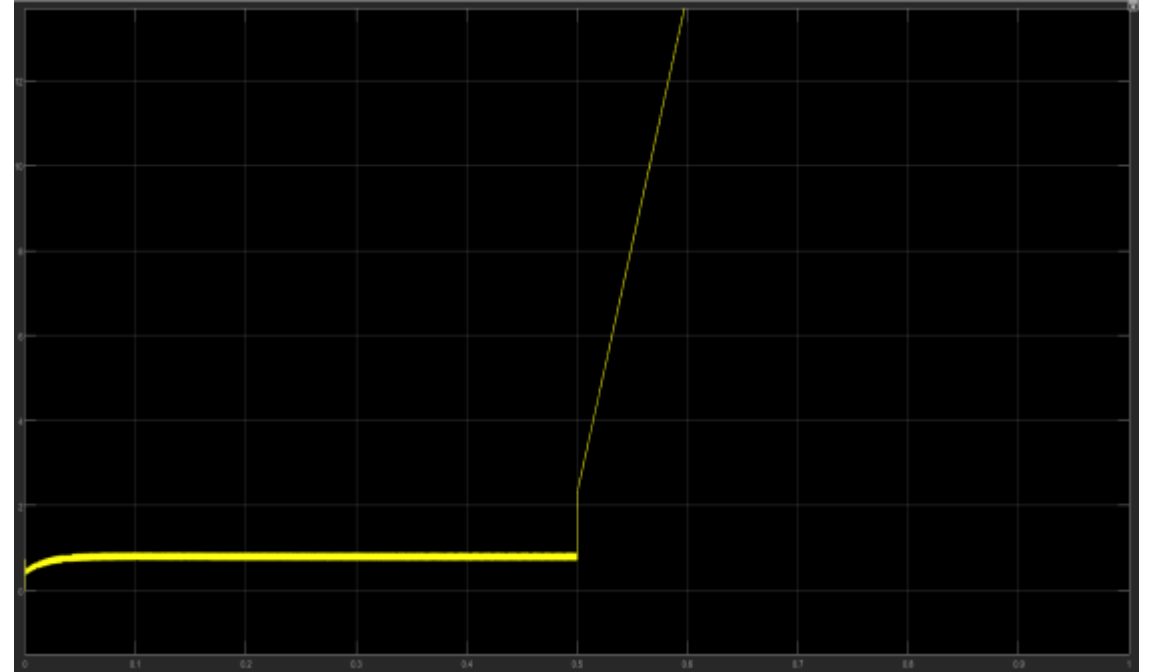


Current Profile

# SHORT CIRCUIT WITH SATURATION BLOCK

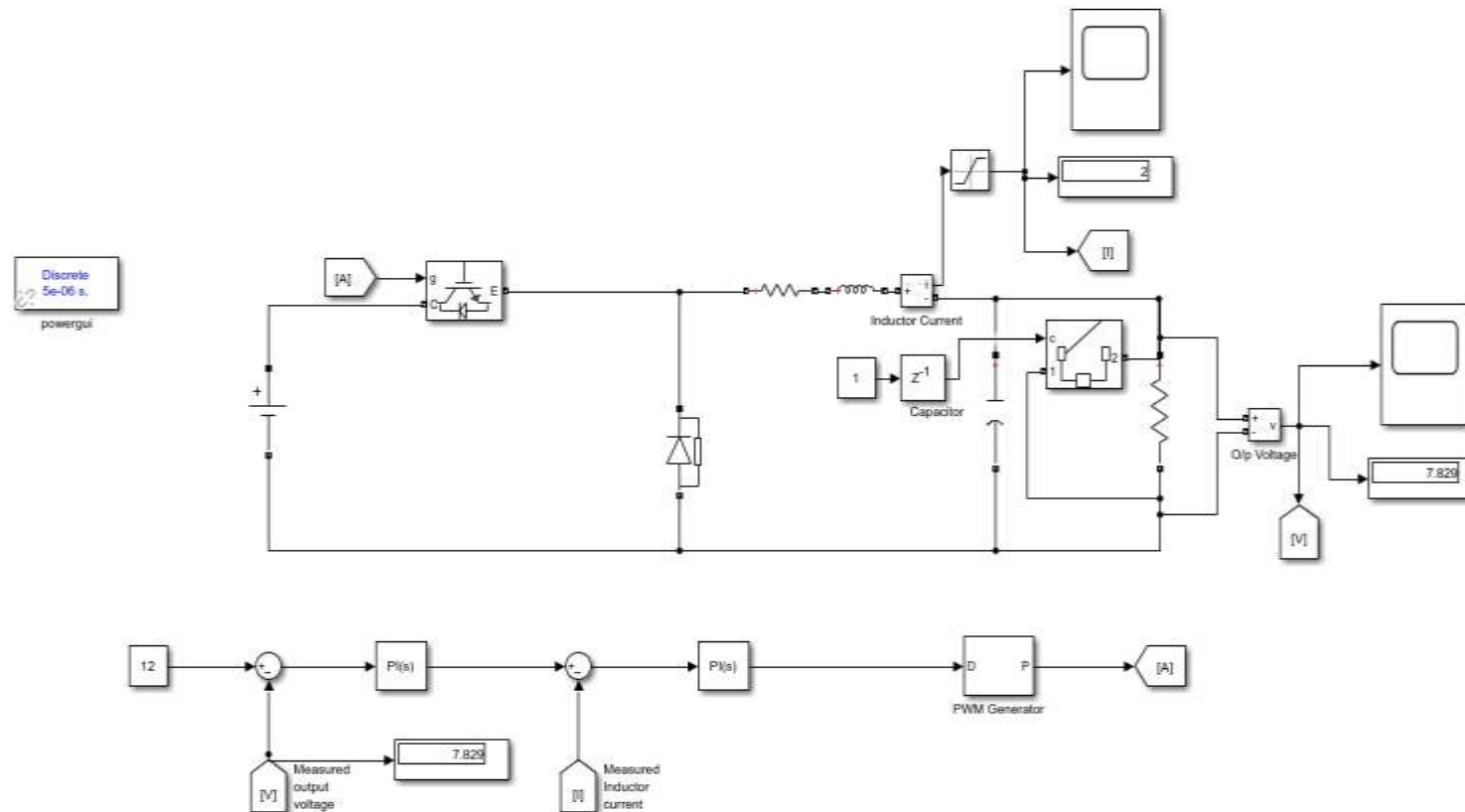

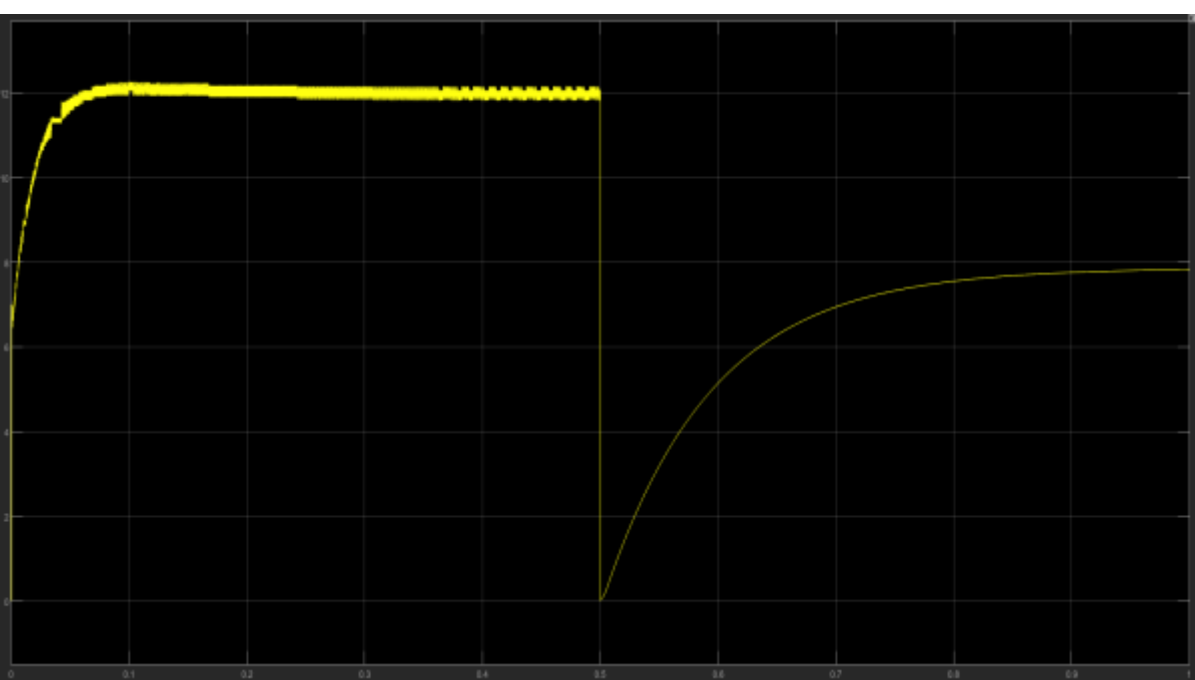


*Voltage Profile*

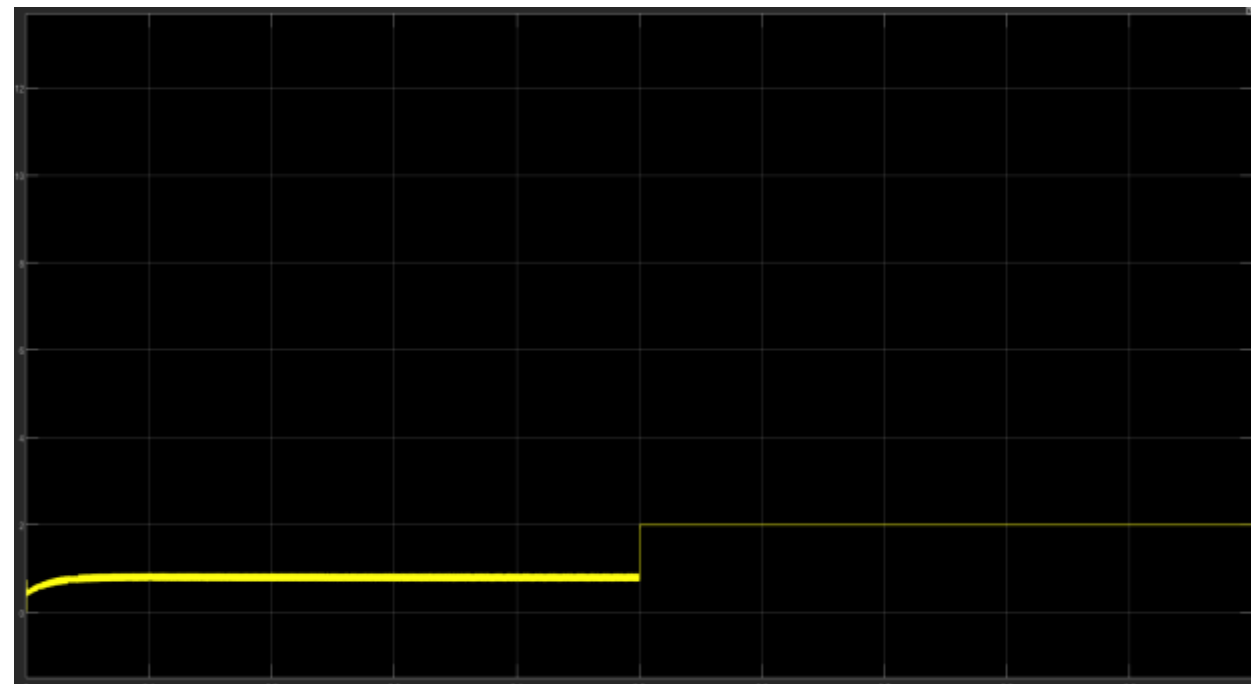

Current Profile
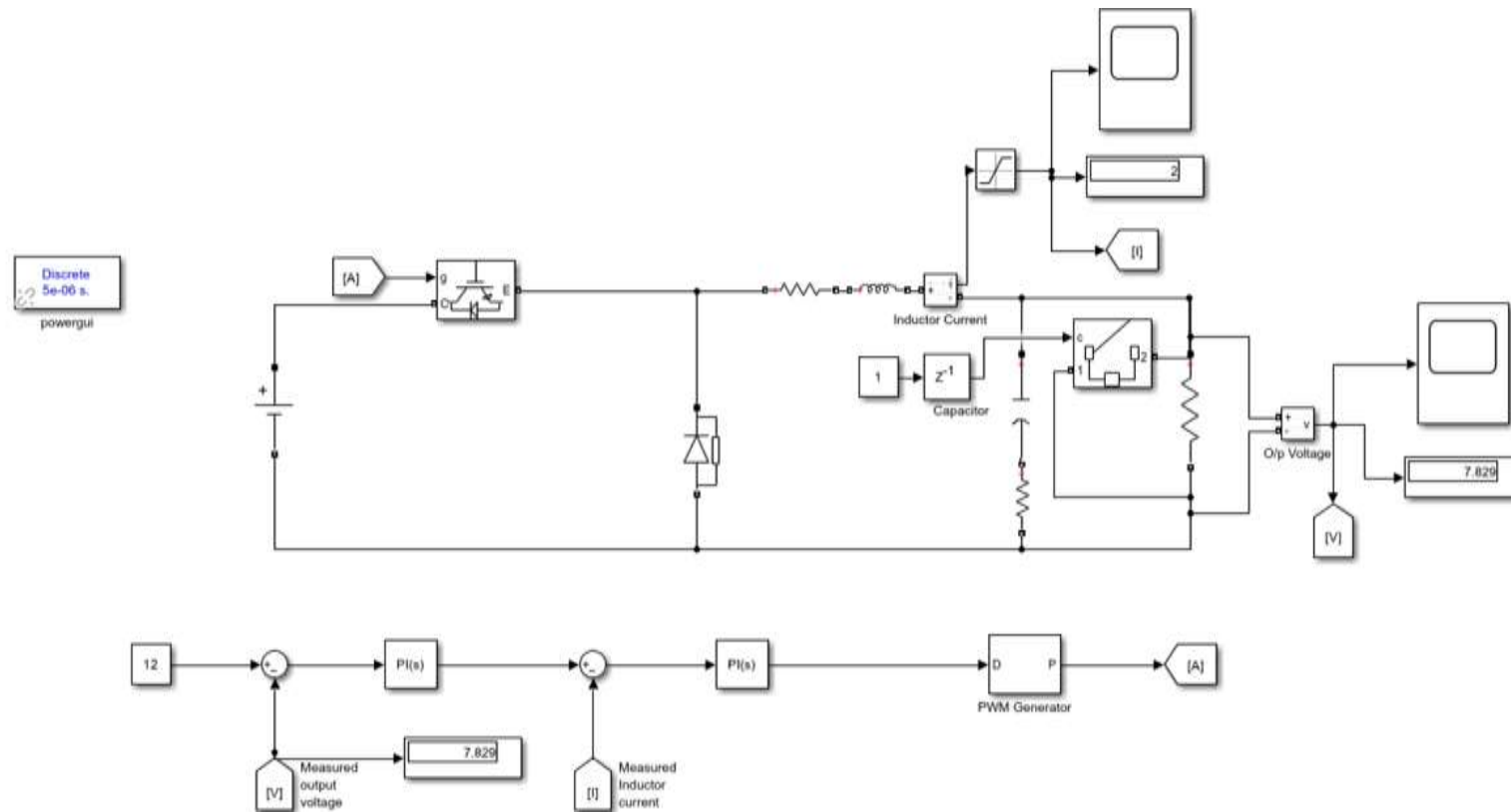
# Resistance variation and show the limits of the Capacitor series resistance variation for stable operation.



\n Transfer Function of iL/d::

$$V_{dc} (L - C R_c R_l)$$

$$\frac{2}{C L (R + R_c)} \left| s + \frac{L + R_l}{C L (R + R_c)} + \frac{R_l s (L + C R R_c)}{2 C L (R + R_c)} \right|$$

\n Transfer function of open loop:

$$V_{dc} \frac{(k_i + k_p s)}{k_{pp} + \frac{k_{ii}}{s}} = (L - C R_c R_l)$$

$$L^2 s^2 + L V_{dc} k_i + L R_l s + L R_l s^2 + C L^2 R s^3 + C L^2 R_c s^3 + L V_{dc} k_p s - C R_c R_l V_{dc} k_i + C R R_c R_l s^2 - C R_c R_l V_{dc} k_p s$$

Expression with "Rc" factored out from the denominator:

$$\frac{(C_{R1} V_{dc} k_{ii} + C_{R1} V_{dc} k_{ii} k_p s + C_{R1} V_{dc} k_{ii} k_{pp} s^2 + C_{R1} V_{dc} k_p k_{pp} s^2) R_c - L V_{dc} k_{ii} - L V_{dc} k_{ii} k_p s - L V_{dc} k_{ii} k_{pp} s^2 - L V_{dc} k_p k_{pp} s^2}{(-C_{L1} s^4 - C_{R1} R_{L1} s^3 + C_{R1} L V_{dc} k_p s^2 + C_{R1} L V_{dc} k_{ii} s) R_c - L^2 s^2 - L R_{L1} s - L R_{L1} s^3 - L V_{dc} k_p s - C_{L1} R_{L1} s^4 - L V_{dc} k_{ii} s}$$


\n Capacitor series resistance Added!!

\n Transfer function with controller::

pop =

$$\frac{2.5\text{e-}13 \text{ s}^4 + 1.875\text{e-}05 \text{ s}^3 - 5.4\text{e-}08 \text{ s}^2 - 0.003054 \text{ s}}{3.75\text{e-}12 \text{ s}^4 + 5\text{e-}06 \text{ s}^3 + 9.33\text{e-}06 \text{ s}^2 + 0.2443 \text{ s}}$$

Continuous-time transfer function.

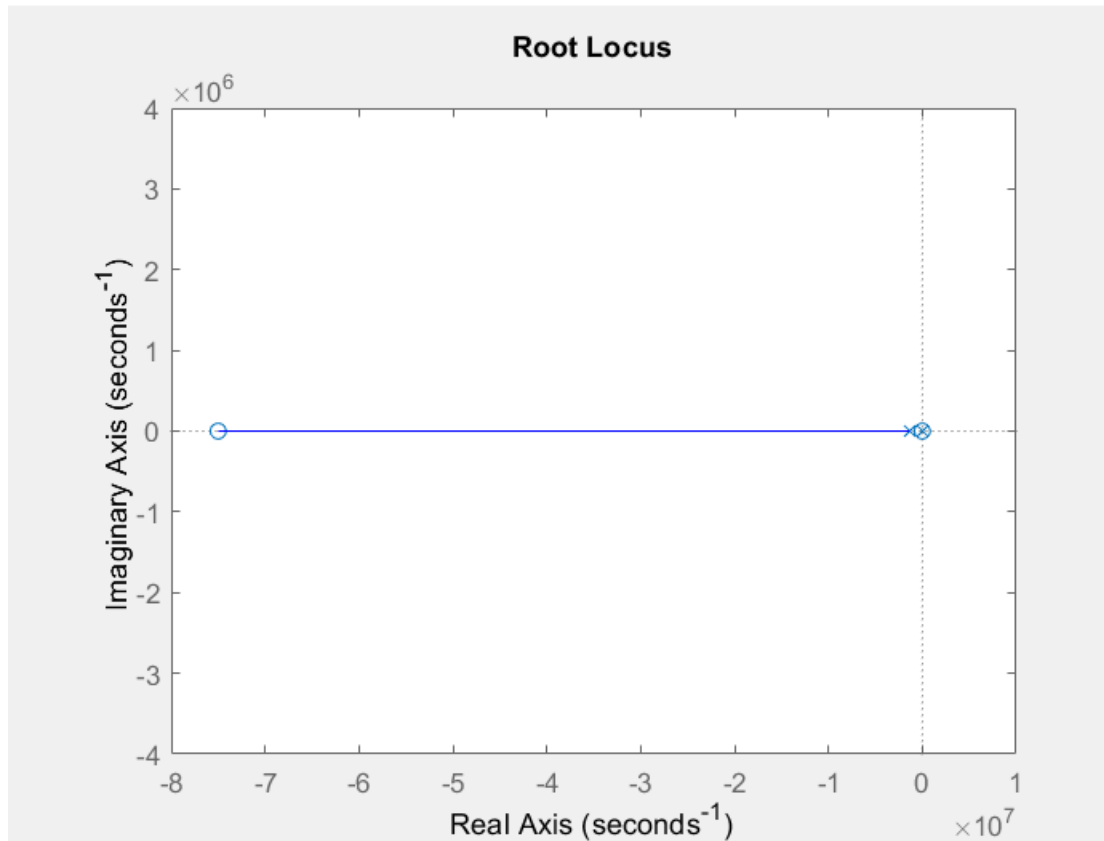

```
clear all;clc;
Vdc=48;
R=15;
L=100e-6;
C=25e-6;
r=0.05;
n = [Vdc/L Vdc/(R*L*C)];
d=[ 1 1/(R*C) 1/(L*C)];
t = tf(n,d); % (iL/d) wo PI
n_1=[Vdc/(L*C)];
d_1=[1 1/(R*C) 1/(L*C)];
t_1=tf(n_1,d_1); % Vo/d wo PI
disp('\n Transfer Function without PI controller:');
flag= (t_1)/t % Vo/iL wo PI
kp_i= [0.0009];
a=50.90;
m = [1 0];
ki_i= a*tf(1,m);
c= kp_i+ki_i;
t_11=t*c; % iL/d w PI inner loop
In= t_11/(t_11+1);
kp_o= [0.08];
p =704.03;
m_1 = [1 0];
ki_2= p*tf(1,m_1);
c_2= kp_o+ki_2;

Num = [((L^2)*C) (C*R*r) (-(C*r*Vdc*(kp_i))) (-(C*r*Vdc*(50.90))) 0];
den = [(R*(L^2)*C) (L*r) ((L^2)+(L*r)+(L*Vdc*(kp_i))) (L*Vdc*(50.90))];
disp('\n Transfer function with controller:');
pop=tf(Num,den)
rlocus(pop);
```

# REFERENCE

---

- [1] Hasan Sucu, Taner Goktas, Muslum Arkan ,“Design, Simulation and Application of Buck Converter with Digital PI Controller ”,Balkan journal of electrical & computer engineering, Vol. 9, No. 2, April 2021.
- [2] P.C. Sen, Zaohong Yang, “DC-TO-DC buck Converters with novel current mode control” , 1999 IEEE

---

*THANK YOU*

